

---

## Contents

<b>Kirchoff's laws</b>	<b>2</b>
Background . . . . .	2
Kirchoff Current Law . . . . .	2
Terms . . . . .	2
Sign Convention . . . . .	3
Statement . . . . .	3
Kirchoff's Voltage Law . . . . .	3
Sign Convention . . . . .	3
Kirchoff's Voltage Law . . . . .	3
<b>Wheatstone Bridge</b>	<b>4</b>
Principle . . . . .	4
Application . . . . .	4
Construction . . . . .	4
Description . . . . .	5
<b>Meter Bridge</b>	<b>5</b>
Definition . . . . .	5
Principle . . . . .	5
Construction . . . . .	5
Working . . . . .	6
Operation . . . . .	6
Calculation . . . . .	6
<b>Potentiometer</b>	<b>6</b>
Definition . . . . .	7
Principle . . . . .	7
Construction . . . . .	7
Calculation of internal resistance of cell . . . . .	7
Setup . . . . .	7
Operation . . . . .	8
Calculation . . . . .	8
Comparison of <i>e.m.f.</i> of two cells. . . . .	9
Setup . . . . .	9
Operation . . . . .	9
Calculation . . . . .	10

---

<b>Conductors</b>	<b>10</b>
Super Conductors . . . . .	10
Mechanism of superconductivity . . . . .	10
Critical Temperature in Super Conductors $T_C$ . . . . .	10
Types of super conductors . . . . .	11
Perfect conductors . . . . .	11
Distinction between perfect conductors and superconductors . . . . .	11
<b>Galvanometer</b>	<b>11</b>
Galvanometer . . . . .	12
Voltmeter . . . . .	12
Multiplier . . . . .	12
Ammeter . . . . .	12
Shunt . . . . .	12
Conversion of galvanometer to voltmeter . . . . .	12
Structure of Circuit . . . . .	13
Calculation . . . . .	13
Conversion of galvanometer to ammeter . . . . .	13
Structure of circuit . . . . .	13
Calculation . . . . .	13

## Kirchoff's laws

**Objective:** *Understand Kirchoff's laws as well as use it calculate unknown parameters in circuits.*

### Background

- The essence of **kirchoff's laws** is due to the fact that calculation across *multi loop* and *multi source* circuits are limited by **Ohm's law**.

### Kirchoff Current Law

#### Terms

- **Junction** is a point in electric circuit where at least **three** electrical nodes are *connected*.

---

## Sign Convention

- **Outgoing** current are taken as **negative**.
- **Incoming** current are taken as **positive**.

## Statement

- **Kirchoff's Current law** states that *algebraic* sum of **incoming** and **outgoing** current in a junction is **0**.

$$\sum I = 0$$

- **Kirchoff's Current Law** is based on *principle* of **conservation of charge**.

## Kirchoff's Voltage Law

### Sign Convention

#### Resistor:

- The **algebraic** sign of voltage in a circuit resistor is **positive** if the direction of **observer** and current is opposite.
- The **algebraic** sign of voltage in a circuit resistor is **negative** if the direction of **observer** and current is same.
- This convention is chosen as **current flows** from **positive** to *negative* direction.

#### Source:

- The **algebraic** sign of voltage in a circuit source is **positive** if the direction of **observer** and current is same.
- The **algebraic** sign of current in a circuit source is **negative** if the direction of **observer** and current is opposite.
- This convention is chosen as **current flows** from **high potential** to *low potential* direction.

## Kirchoff's Voltage Law

- **Kirchoff's** Voltage Law states that the **algebraic** sum of change in *potential* around a circuit is **0**.

$$\sum \Delta V = 0$$

- 
- **Potential** includes the **terminal p.d.** and **emf** of source.
  - **Kirchoff's Voltage Law** is base on the **principle of conservation of energy**.

## Wheatstone Bridge

**Objective:** *Describe the circuit diagram and working of wheatstone bridge circuit and understand its importance in real situation.*

### Principle

- The principle of **wheatstone bridge circuit** states that , the product of resistances in opposite arms is equal in a circuit arranged in the form of a **quadilateral** when *current* flowing in between **the diagonal** of circuit is **0**.

### Application

- Wheatstone bridge circuit can be used to find the **unknown** electrical resistance in a circuit if other 3 resistances arranged in the quadilateral are known.
- If  $R, P, Q, X$  are the resistances arranged serially in a circuit then,

$$PX = RQ$$

$$X = \frac{Q}{P}R$$

### Construction

- A circuit is arranged in the form of a **quadilateral**  $ABCD$  .
- A **source** is present between  $A$  and  $C$  .
- A **galvanometer** is present between  $B$  and  $D$  .
- Two resistances of **known** parameter are placed between  $A$  and  $B$  and between  $B$  and  $C$  .
- A resistance box or a **variable** resistor is placed between  $A$  and  $D$  .
- The **unknown** resistance to be calculated is placed between  $D$  and  $C$  .

---

## Description

- The *wheatstone bridge* is said to be **balanced** when *current* through  $B$  and  $D$  is **0**.
- This is **shown** by **null deflection** of the galvanometer.
- The **null deflection** is achieved by *adjusting* the value of **resistance** of the **variable** resistor.

## Meter Bridge

**Objective:** *Describe meter bridge and understand it.*

### Definition

- **Meter bridge** is a *simple* circuit used to **measure** and **compare** resistances and hence **resistivity**.
- It is *described* as an **application** of **wheatstone bridge**.

### Principle

- **Meter bridge** is based on the **principle of wheatstone bridge**.

### Construction

- *Circuit elements* of **meter bridge** are:
  1. A **wire** having *length* of  $100\text{cm}$  as  $AC$ .
  2. Two *L shaped* **brass** plates between  $A$  and  $B$  and between  $B$  and  $C$ .
  3. After each **brass** plate there is a **gap** to reach at point  $B$ .
  4. A **resistance box**  $R$  is placed between gap  $B$  and  $C$ .
  5. A **unknown resistor**  $X$  is placed between gap  $A$  and  $B$ .
  6. A **galvanometer** is connected at point  $B$  with its one **terminal** connected to a **jockey**.

---

## Working

### Operation

- A **resistance**  $R$  is setup across  $B$  and  $C$  by the *resistance box*.
- The jockey is slide over the **wire**  $AC$  to **null point** by **null deflection** of *galvanometer*. at point  $D$ .

### Calculation

#### Variables:

- Length of segment  $AD = l$
- Resistance of segment  $AD = \rho \frac{l}{A}$
- Length of segment  $DC = 100 - l$
- Resistance of segment  $DC = \rho \frac{100-l}{A}$

According to the principle of **Wheatstone bridge**,

$$X \rho \frac{100-l}{A} = R \rho \frac{l}{A}$$

$$X = \frac{l}{100-l} R$$

- If  $L$  is the length of resistor  $X$  and  $A$  is the cross section area, **resistivity** can be *calculated* by:

$$\rho = X \frac{A}{L}$$

- Comparison of **resistances** of *resistors* can be done by replacing  $R$  with an unknown resistance  $X_2$  and considering another *unknown* resistance between  $A$  and  $B$  as  $X_1$ .

$$\frac{l}{100-l} = \frac{X_1}{X_2}$$

## Potentiometer

**Objective:** *Know construction, working and importance of potentiometer*

---

## Definition

- **Potentiometer** is a *circuit* that is used to determine **emf** or **terminal p.d.**.

## Principle

- **Potentiometer** is based on the principle of *uniform* decrease in **p.d.** across a length.
- In a **steady** current the **potential difference** across a *portion* of wire is directly proportional to it's **length**.

$$V \propto l$$

$$V = IR$$

$$R = \rho \frac{l}{A}$$

$$V = \frac{I\rho}{A}l$$

- If steady current  $I$  flows in a wire of uniform **length**  $l$  ,

$$V = kl$$

- $k$  is termed as **potential gradient** or **constant of potentiometer**.

## Construction

- The **circuit elements** of a *potentiometer* circuit are:
  1. A **driver's source**  $E_{DV}$  to provide *steady current* known as an *accumulator*.
  2. A **rheostat** to maintain *current* across the *circuit*.

## Calculation of internal resistance of cell.

### Setup

- The **circuit elements** of the setup *apparatus* are:
  1. A **driver's source** whose *positive terminal* is attached at a point  $A$ .

- 
2. A cell of emf  $E$  whose *positive* terminal is attached to a point  $A$  with **internal resistance**  $r$ .
  3. A resistance box of **resistance**  $R$  connected in parallel with the cell of emf  $E$
  4. A switch  $k_1$  in series with *resistance box*.
  5. A **galvanometer** connected to the *negative* terminal of the *cell* whose one end is equipped with a **jockey**.

### Operation

#### Keeping $k_1$ open:

- The **jockey** is slid over the wire  $AB$  to obtain null point  $C$ .
- The length  $AC$  is  $l_1$ .

#### Keeping $k_1$ closed:

- The **jockey** is slide over the wire  $AB$  to obtain null point at  $D$ .
- The length  $AD$  is  $l_2$ .

### Calculation

$$V_{AC} = E$$

$$E = kl_1$$

$$V_{AD} = V$$

$$V = kl_2$$

Further,

$$I = \frac{E}{r}$$

$$V = I \frac{Rr}{R+r}$$

$$V = \frac{ERr}{r(R+r)}$$

$$R+r = \frac{ER}{V}$$

$$r = \left( \frac{E}{V} - 1 \right) R$$

- The **internal resistance** of the cell is give by:



---

$$r = \left(\frac{l_1}{l_2} - 1\right)R$$

### Comparison of *e.m.f.* of two cells.

#### Setup

- The **circuit elements** of the setup *apparatus* are:
  1. A **driver's source** whose *positive terminal* is attached at a point *A*.
  2. A cell of emf  $E_1$  whose *positive terminal* is attached to a point *A*.
  3. A cell of emf  $E_2$  connected in parallel with the cell of *emf*  $E_1$
  4. A switch  $k_1$  in series with the cell e.m.f  $E_1$ .
  5. A switch  $k_2$  in series with the cell of e.m.f.  $E_2$ .
  6. A **galvanometer** connected to the *negative terminal* of the *cell* whose one end is equipped with a **jockey**.

#### Operation

##### Keeping $k_1$ open and $k_2$ closed:

- The **jockey** is slid over the wire  $AB$  to obtain null point  $C$  .
- The length  $AC$  is  $l_1$  .

##### Keeping $k_1$ closed and $k_2$ open:

- The **jockey** is slide over the wire  $AB$  to obtain null point at  $D$  .
- The length  $AD$  is  $l_2$  .

#### Cases:

- $E_1 > E_2 \implies l_1 > l_2$
- $E_1 < E_2 \implies l_1 < l_2$

---

## Calculation

$$E_{AC} = kl_1$$

$$E_{AD} = kl_2$$

- Dividing the **equations** , the relation of comparison is:

$$\frac{E_{AC}}{E_{AD}} = \frac{l_1}{l_2}$$

## Conductors

### Objective:

1. Understand the concept of super conductors.
2. Know the meaning of perfect conductors and distinguish it from super conductors.

## Super Conductors

- **Superconductors** are elements, alloys or materials that conduct electricity with zero resistance in below a certain *temperature* .
- **Superconductors** can sustain *electrons* across the circuit without needing any **emf** after setting up the electrons initially .

### Mechanism of superconductivity

- **Superconductivity** occurs by the principle of **phonon** mediated **cooper pairs**.
- **Two** electrons pair to *mutually* traverse the lattice, against the *electrostatic* repulsion.
- **Electrons** are bounded together by binding energy from *net attractive* force which is in the *order of millivolts* .

### Critical Temperature in Super Conductors $T_C$

- **Critical temperature** is a particular value of *temperature* below which the *material* exhibits **superconducting** property.

---

## Types of super conductors

- **Type I** superconductors are those that exhibit superconducting property by:
  - Formation of **Cooper Pairs** .
  - Shifting to **normal** conducting phase by **destruction** of superconducting phase after application of **magnetic field** larger than *critical magnetic field* .
  - Consist of single **elements** only.
  - Mercury, Lead are *examples* of these conductors.
- **Type II** superconductors are those that exhibit superconducting property by:
  - Consists of materials commonly **alloys** .
  - Common **materials** include 3 *oxygen* atoms for each two *metal* atoms.
  - Can carry **small** amounts of current and behave as super conductors even when there is application of **magnetic field** exceeding critical magnetic field.

## Perfect conductors

- **Perfect conductors** are those that have **infinite** conductivity or **zero** resistivity.
- **Perfect conductors** can maintain current in a circuit without requiring sustaining **source** in the circuit.
- The **magnetic field** applied in such conductor has no effect in changing the ability of the **conductor** to conduct *electricity* .

## Distinction between perfect conductors and superconductors

- **Superconductors** are a victim to *quantization of magnetic flux* and *Meissner effect* .
- There is no **magnetic field** inside superconductors while perfect do.
- **Superconductors** are practical whilst **perfect conductors** are hypothetical and ideal description.

## Galvanometer

**Objective:** *Learn the technique to convert galvanometer into voltmeter and ammeter.*

---

## Galvanometer

- **Galvanometer** is sensitive instrument that *detects* feeble currents in a circuit.
- **Galvanometer** has low resistance.
- It is equipped with a **pointer** to show deflection on flow of **current** .

## Voltmeter

- **Voltmeter** is an electrical instrument that measures **potential** difference in a circuit.
- **Voltmeter** has very high resistance.

## Multiplier

- **Multiplier** is a component of electrical circuit that has **large** resistance.
- **Multiplier** is used to decrease current in a circuit by **decreasing** resistance.

## Ammeter

- **Ammeter** is an electrical instrument that measures **current** in an electrical circuit.
- **Ammeter** has very *low* resistance.

## Shunt

- **Shunt** is a component of electrical circuit that has very low *resistance* .
- **Shunt** is used to increase current in **electric** circuits by increasing **resistance**.

## Conversion of galvanometer to voltmeter

- A **galvanometer** is converted into a voltmeter by adding *multiplier* in **series** in the circuit.

---

### Structure of Circuit

- The *electrical* components in the circuit are:
  1. A galvanometer having **resistance**  $G$  .
  2. A **multiplier** having **resistance**  $R$  .

### Calculation

- The same **current**  $I_g$  flows through galvanometer and **multiplier**

$$V = V_R + V_g$$

$$V = I_g R + I_g G$$

$$I_g R = V - I_g G$$

$$R = \frac{V}{I_g} - G$$

- Evaluation of the **total** resistance in the circuit to give **resistance** of new voltmeter yields:

$$R_{total} = R + G$$

### Conversion of galvanometer to ammeter

- A **Galvanometer** is converted into a ammeter by adding shunt in parallel with the **galvanometer** in the circuit.

### Structure of circuit

- The **electrical** components in the circuit are:
  1. A galvanometer of resistance  $G$  .
  2. A **shunt** connected parallel with the galvanometer of resistance  $S$ .

### Calculation

- The *p.d.* across both the galvanometer and shunt is same.

---

$$V_g = V_s$$
$$I_g G = (I - I_g) S$$

$$S = \frac{I_g G}{I - I_g}$$

- Effective resistance of the shunt and galvanometer to give **resistance** of *new* ammeter is:

$$R_{total} = \frac{SG}{S + G}$$